

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, Dec 2019

Programme Name: B. Tech-Electronics Communication Engineering

Semester : III

Course Name : Network Analysis

Time : 03 Hrs.


Course Code : ECEG-2020

Max. Marks : 100


Nos. of page(s) : 3


Instructions: Attempt all the sections.


SECTION A (20 Marks)


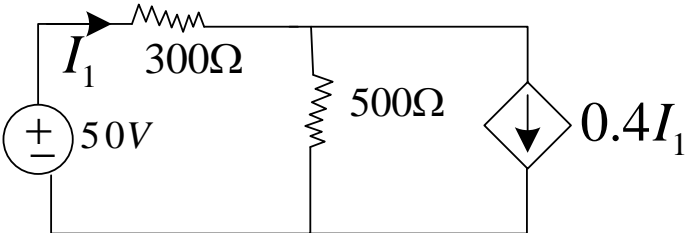
S. No.	Attempt all the questions.	Marks	CO
Q 1	For the circuit use loop analysis to find I_1 and the power absorbed by the $500\ \Omega$ resistor.  Fig. (1)	5	CO1
Q 2	Define Y-parameters. Determine the relationship between the Z and Y parameters.	5	CO2
Q 3	Define the following terms: (i) Mesh and loop (ii) Path (iv) Planar and non-planar graph	2+2+1	CO4
Q 4	What are the positive real functions? And write its properties.	5	CO3

SECTION B (40 Marks)

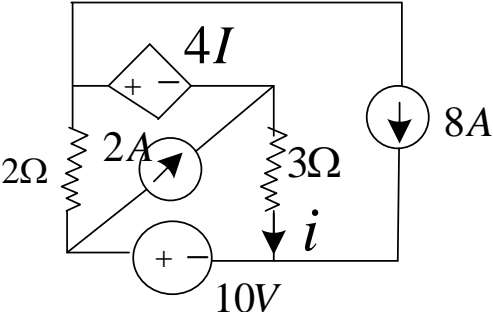Attempt all the questions.			
Q 5	Find the current in the circuit shown in Fig (2). Using the superposition theorem.  Fig. (2)	10	CO1

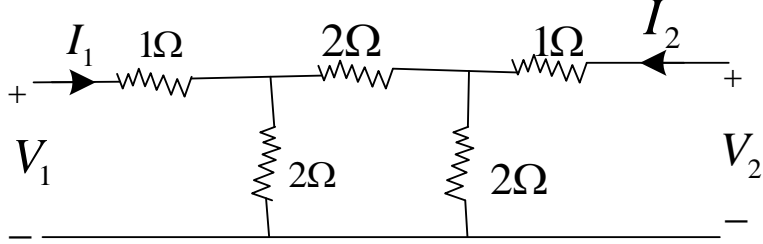Q 6	<p>For the network shown in Fig. (3) determine the ABCD parameters</p>  <p style="text-align: right;">Fig. (3)</p>	10	CO2
-----	---	-----------	------------

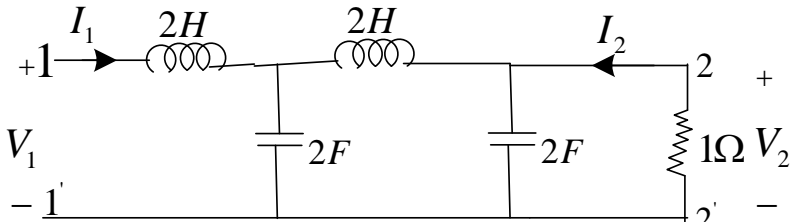Q 7	<p>Find the transfer ratio $\left(\frac{V_2}{V_1}\right)$ of the network shown in Fig. (4),</p>  <p style="text-align: right;">Fig. (4)</p>	10	CO3
-----	---	-----------	------------

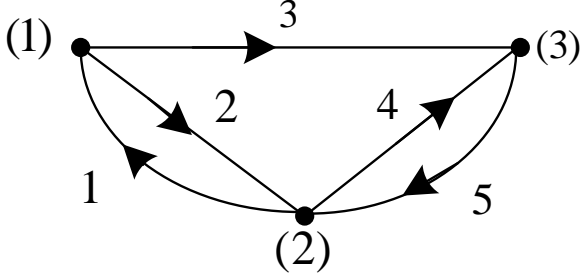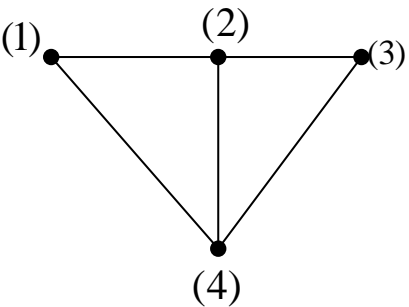Q 8	<p>Attempt both the parts:</p> <p>(a) In the tree link graph of Fig. (5), develop the fundamental cut-set matrix and equilibrium equations using nodal analysis.</p>  <p style="text-align: center;">Fig. (5)</p> <p>(b) Figure (6) represents a graph of a network. Show the total number of tree, twigs and links.</p>  <p style="text-align: center;">Fig. (6)</p>	10	CO4
-----	---	-----------	------------

SECTION-C (40 Marks)

Q 9

Attempt both the parts:

(A) Find the open circuit driving point impedance at terminals 1-1' of the ladder work shown in Figure (7).

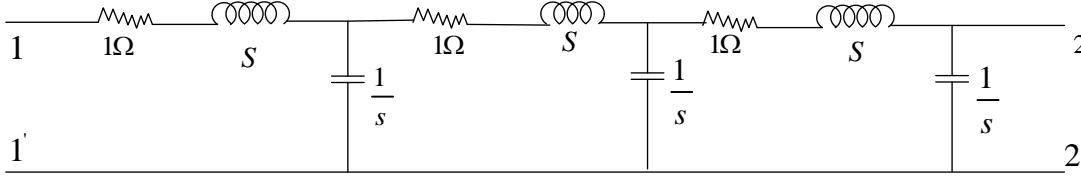


Fig. (7)

(B) Determine the load current using Millman's theorem. Network shown in Fig. (8)

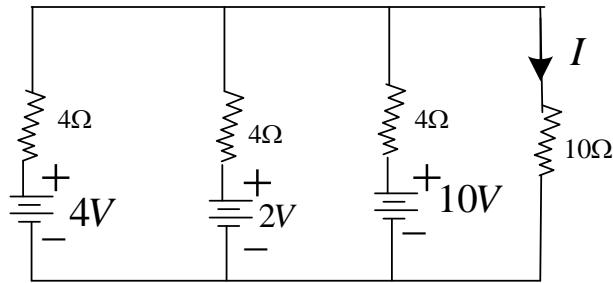


Fig. (8)

10+10

**CO3,
CO1**

Q 10

An impedance function is given by

$$Z(S) = \frac{S(S + 2)(S + 5)}{(S + 1)(S + 4)}$$

Find the R-L representation of (a) Foster- I and II forms (b) Cauer –I and II forms

20

CO4