Name:

**Enrolment No:** 



## UNIVERSITY OF PETROLEUM AND ENERGY STUDIES End Semester Examination, December 2022

Course: Electric Vehicle and Battery Management System Program: B. Tech (Automotive Design Engineering) Course Code: MEAD 3013

Semester : V Time : 03 hrs. Max. Marks: 100

Instructions: All section questions are compulsory.

SECTION A (50x4M=20Mark)			
S. No.	Marks	СО	
Q 1 List out advantages of fuzzy logic based energy management control strategy in electric and hybrid vehicles?	4	CO1	
Q 2 What is the significance of a communication network in EVs? Explain the functions of the in-vehicle communication network.	4	CO1	
Q 3 Define the configuration of v/f controlled induction motor drive with field weakening mode and constant-torque mode.	4	CO2	
Q 4 Explain the power flow control modes for a series-parallel hybrid vehicle.	4	CO3	
Q 5 Explain the four-quadrant chopper control of DC motor.	4	CO2	
SECTION B			
(4Qx10M= 40 Marks)			
Q 6 Define SOB with active and passive circuit approach. Also explain the significance of the each methods used.	10	CO5	
Q 7 Describe the terms State-of-Charge, Depth-of-Discharge, and State of Health as applied to lithium ion batteries used in the electric vehicles.	10	CO3	
Q 8       An electric vehicle has motor rating of 50kW, and battery pack rating is 20kWh. Calculate following parameters:       (i) Is it possible to drive 200 km range considering vehicle weight 800 Kg and maximum speed of 65 Km/h, Justify with proper parameters?         (ii) Calculate current with 0.5C, 1C and 5C rate.       (iii) What is the electrical motor power output if the total efficiency of power converter and motor combination is 96%.         (iv) What is the maximum power that can be transmitted to the wheels if the transmission efficiency is 94%?         OR         Draw the block diagram of a general Fuzzy Logic Controller (FLC) and show the core components of the FLC and the inputs and outputs relevant to a hybrid electric vehicle control.	10	CO4	

Q 9 With neat diagram explain the operation of full wave phase controlled rectifier with RLE load with suitable waveforms for electric vehicles.	10	CO3	
SECTION-C (20x20M-40 Marks)			
Q 10 A 12V battery pack is connected to series RL load with L=100mH. The battery pack has rated capacity of 120Ah. At t=0 switch is closed and the battery begins to discharge.			
<ul> <li>a) Calculate and plot battery discharge current i(t), if the steady state discharge is C/5. Neglect voltage drop.</li> <li>b) Calculate and plot SoC, assuming that t=0, the battery is charged to rated capacity.</li> <li>c) Calculate the time according to 70% DoD, assume t&gt;&gt;100ms.</li> </ul>	20	CO5	
Q 11 Design and describe the working of a buck converter/ DC-DC step down converter through the neat circuit diagram and appropriate waveforms of supply voltage, load voltage, load current and voltage across the SCR. OR Design a regenerative braking circuit using step-up chopper used in mild hybrid electric vehicle system is represented with below figure also explain its characteristics with neat sketch. Explain the forward motoring and regenerative (forward) braking control of a DC motor with a single chopper. Give circuit diagram, and show the quadrants of operation.	20	CO4	