

Name:
Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, May 2022

Programme Name: B.Tech Mechatronics
Course Name: Analog & Digital Electronics
Course Code: ECEG 2030
Nos. of page(s): 3

Semester: IV
Time: 03 hrs
Max. Marks: 100

SECTION A
(5Qx4M=20Marks)

S. No.		Marks	CO
1	<p>Evaluate the expression of the output voltage V_o for the given OPAMP circuit shown in Figure 1?</p> <div style="text-align: center;"> <p>Figure 1</p> </div>	4	CO3
2	<p>Convert the following numbers into the corresponding number system .</p> <p>A. $(88)_{10} = (?)_{16}$ B. $(1101.101100)_2 = (?)_{16}$ C. $(162)_8 = 10$</p>	4	CO1
3	<p>The overall gain of a multistage amplifier is 140. When negative voltage feedback is applied, the gain is reduced to 17.5. Find the fraction of the output that is fed back to the input (feedback gain).</p>	4	CO1
4	<p>Illustrate the applications of the oscillators?</p>	4	CO2
5	<p>Define the “Barkhausen criterion” for sustained oscillations?</p>	4	CO2

SECTION B
(4Qx10M= 40 Marks)

6	<p>For the given CE BJT configuration as shown in Figure 2, evaluate the DC operating Points (I_{CQ}, V_{CEQ}) and also comment on its operating region?</p>	10	CO1
---	--	----	-----


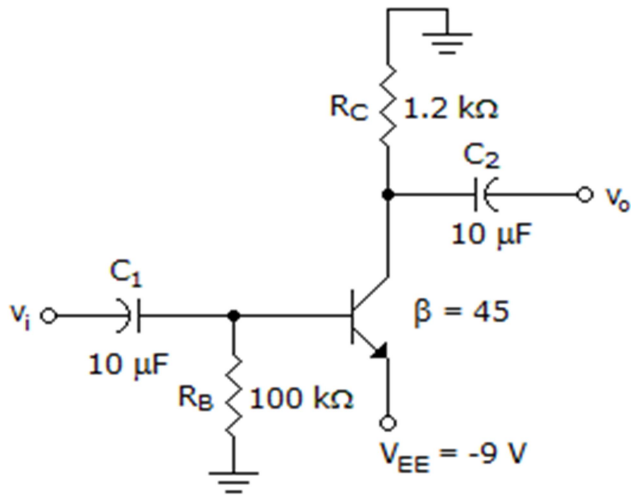
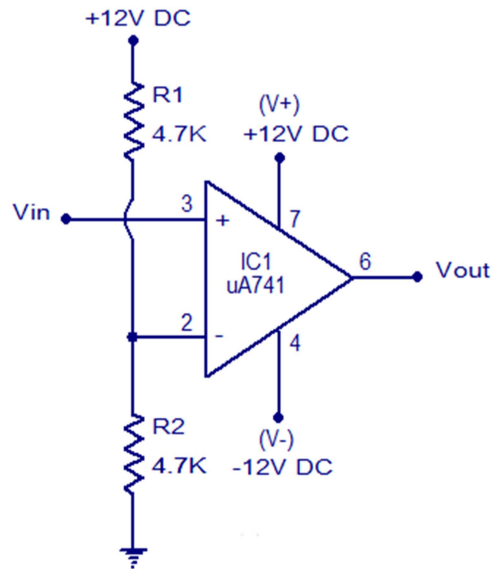


Figure. 2

7

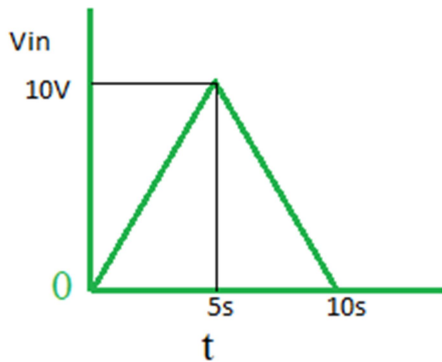Consider the given OPAMP network as shown in Figure. 3 and sketch the V_{OUT} waveform with proper explanation and working?



10

CO2

Figure. 3

8

Implement the 16X1 MUX by using 2X1 MUX.

10

CO3

9

Implement the 4 bit up counter by using T flip flop for number of states =16.

OR

10

CO2

Develop a full adder using two half adders. Support your combinational circuit with the help of a truth table?

SECTION-C
(2Qx20M=40 Marks)

10 Implement the following Boolean function: $F(A, B, C) = A'B'C + AB + AB'C$ by using only one MUX with suitable number of inputs. 20 CO4

11 Derive the relation for frequency of sustained oscillations to design the Wien bridge oscillator for figure 6.. Illustrate the nature of oscillations if $R_2 = 4R_1$ and $R_2 = 0.5 R_1$. Draw neat sketch of the waveform for all the cases.

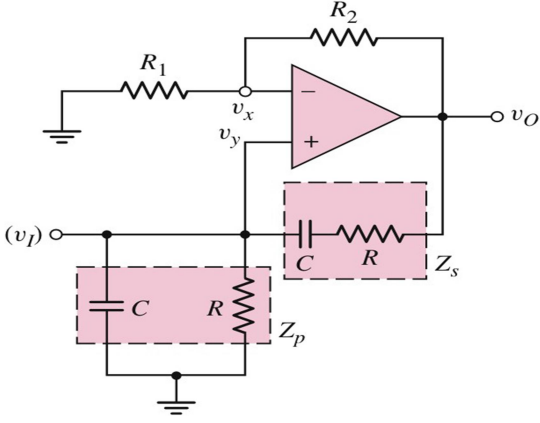


Figure. 4

OR

Evaluate the following for the given schematic below (Figure .5)
 (assume $h_{ie} = 20k$)
 (a) Calculate Z_i and Z_o .
 (b) Find A_v and A_i .
 (c) For $V_i = 500mV \cdot \sin 250t$ plot the output voltage waveform V_o ?

20 CO3

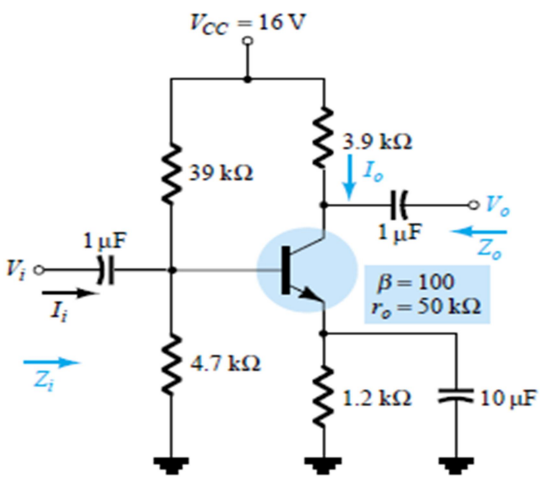


Figure. 5