


Name:			
Enrolment No:			
<b>UPES</b> <b>End Semester Examination, May 2023</b>			
<b>Course: Aircraft Electrical System</b> <b>Program: B.Tech Aerospace Engineering (Avionics)</b> <b>Course Code: AVEG 3002P</b>		<b>Semester: VI</b> <b>Time : 03 hrs.</b> <b>Max. Marks: 100</b>	
<b>Instructions: Attempt all the questions. Assume any missing data. Use of calculator is allowed.</b>			
<b>SECTION A</b> <b>(5Qx4M=20Marks)</b>			
S. No.		Marks	CO
Q 1	How do we achieve voltage and frequency stability in the grid?	4	CO1
Q 2	Briefly explain the working of a dc-dc buck converter along with the output voltage and current waveforms.	4	CO2
Q 3	What is holding and latching current of SCR?	4	CO3
Q 4	What are the limitations of PWM inverters?	4	CO4
Q 5	What are the conditions that must be met to synchronize a generator to the grid?	4	CO1
<b>SECTION B</b> <b>(4Qx10M= 40 Marks)</b>			
Q 6	Explain the performance parameters of a rectifier along with their mathematical expressions.	10	CO5
Q 7	For the single-phase, full-wave, uncontrolled rectifier, the supply voltage is 110V, 50Hz, the load resistor is 25Ω. Calculate: (a) The average value of the output voltage and current. (b) The rms value of the output voltage and current. (c) The dc power consumed by the load ( $P_{dc}$ ) and the average value of the power delivered to the load ( $P_{ac}$ ). Sketch the appropriate voltage and current waveforms	10	CO4
Q 8	Explain the working of single-phase full wave-controlled rectifier connected to a resistive load along with the input and output voltage and current waveforms.	10	CO3
Q 9	Draw and explain the static I-V characteristics of SCR. <b>OR</b> Explain the various triggering methods of thyristor.	10	CO2
<b>SECTION-C</b> <b>(2Qx20M=40 Marks)</b>			

<p>Q 10</p>	<p>A single-phase 230V, 1 kW heater is connected across 1-phase, 230V, 50Hz supply through an SCR. For firing angle delays of <math>45^\circ</math> and <math>90^\circ</math>, calculate the power absorbed in the heater element.</p> <p style="text-align: center;"><b>OR</b></p> <p>A 230V, 50Hz, single-phase half-wave controlled rectifier is triggered at a firing angle of <math>40^\circ</math> and the load current extinguishes at an angle of <math>210^\circ</math>. Find the circuit turn off time, average output voltage and the average load current for</p> <p>(a) <math>R = 5\Omega</math>, <math>L = 2\text{mH}</math>  (b) <math>R = 5\Omega</math>, <math>L = 2\text{mH}</math> and <math>E = 110\text{V}</math>.</p>	<p>20</p>	<p>CO5</p>
<p>Q 11</p>	<p>A dc battery is charged through a resistor <math>R</math> as shown in Fig. 1. Derive an expression for the average value of charging current in terms of <math>V_m</math>, <math>E</math>, <math>R</math> etc. on the assumption that SCR is fired continuously</p> <p>(a) For an ac source of 230V, 50Hz, find the value of average charging current for <math>R = 8\Omega</math> and <math>E = 150\text{V}</math>.  (b) Find the power supplied to battery and that dissipated in the resistor.  (c) Calculate the supply power factor.</p>	<p>20</p>	<p>CO4</p>

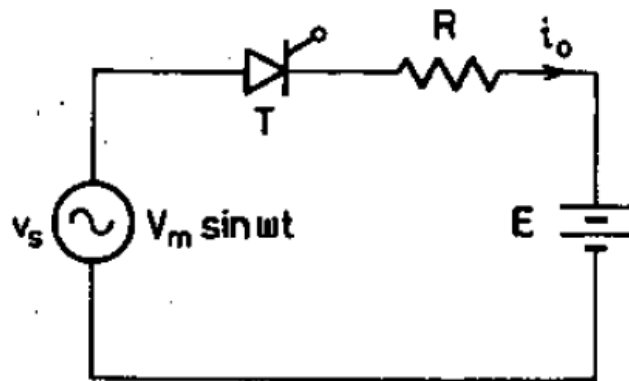


Fig. 1